

# Lecture 10 – K-maps

Dr. Aftab M. Hussain,
Associate Professor, PATRIoT Lab, CVEST

#### Gate level minimization

- Some history: although we use the term Karnaugh map (named after Maurice Karnaugh, 1953) for the map method, it dates back further
- In 1881, Allan Marquand published a paper criticizing "Mr. Venn" for his approach to visualization of logic problems using curvilinear shapes and proposed a method with noninteresting squares
- Non-intersecting because he was concerned with two-state variables that are either true or false

XXXIII. On Logical Diagrams for n terms. By Allan Marquand, Ph.D., late Fellow of the Johns Hopkins University\*.


IN the Philosophical Magazine for July 1880 Mr. Venn has offered diagrams for the solution of logical problems involving three, four, and five terms. From the fact that he makes use of circles, ellipses, and other curvilinear figures, the construction of diagrams becomes more and more difficult as new terms are added. Mr. Venn stops with the five-term diagram, and suggests that for six terms "the best plan would be to take two five-term figures."

It is the object of this paper to suggest a mode of constructing logical diagrams, by which they may be indefinitely extended to any number of terms, without losing so rapidly their special function, viz. that of affording visual aid in the solution of problems.

Conceiving the logical universe as always more or less limited, it may be represented by any closed figure. For convenience we take a square. If then we drop a perpendicular from the middle point of the upper to the lower side of the square, the universe is prepared for a classification of its contents by means of a single logical term.

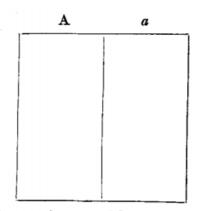
#### Gate level minimization

- Some history: although we use the term Karnaugh map (named after Maurice Karnaugh, 1953) for the map method, it dates back further
- In 1881, Allan Marquand published a paper criticizing "Mr. Venn" for his approach to visualization of logic problems using curvilinear shapes and proposed a method with noninteresting squares
- Non-intersecting because he was concerned with two-state variables that are either true or false





This represents a universe with its A and not-A "compartments." The quantitative relation of the compartments being insignificant, they may for convenience be represented as equal.

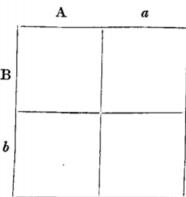The introduction of a second term divides each of the existing compartments. This may be done by a line drawn at right angles to our perpendicular and through its centre, thus:—




- There are four minterms for two variables; hence, the map consists of four squares, one for each minterm
- The map can be drawn to show the relationship between the squares and the two variables x and y
- The 0 and 1 marked in each row and column designate the values of variables
- In minterm form, variable x appears primed in row 0 and unprimed in row 1. Similarly, y appears primed in column 0 and unprimed in column 1

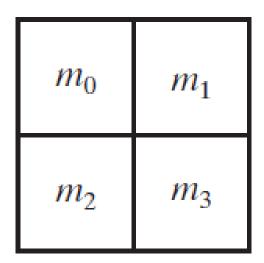


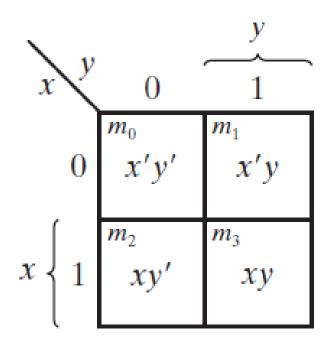


- In 3 variable problems, there are eight minterms for three binary variables; therefore, the map consists of eight squares
- The map is marked with numbers in each row and each column to show the relationship between the squares and the three variables
- For example, the square assigned to  $m_5$  corresponds to row 1 and column 01
- Each cell of the map corresponds to a unique minterm, so another way of looking at the square is  $m_5 = xy'z$
- Note that there are four squares in which each variable is equal to 1 and four in which each is equal to 0

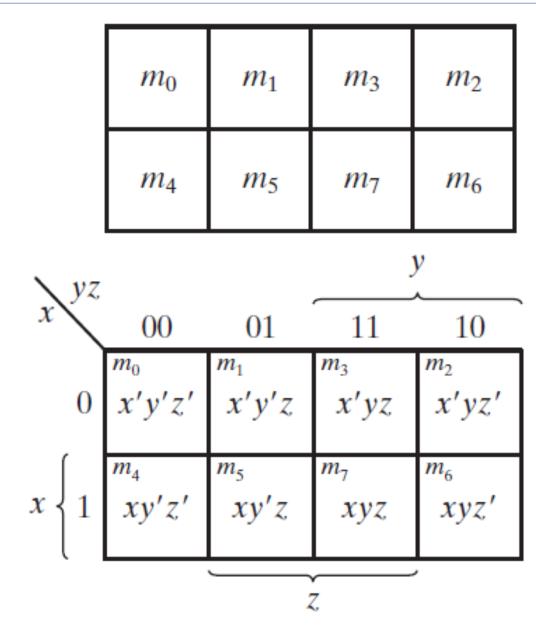

- Here is the magic: To understand the usefulness of the map in simplifying Boolean functions, we must recognize the basic property possessed by adjacent squares: Any two adjacent squares in the map differ by only one variable, which is primed in one square and unprimed in the other
- For example,  $m_5$  and  $m_7$  lie in two adjacent squares
- Variable y is primed in  $m_5$  and unprimed in  $m_7$ , whereas the other two variables are the same in both squares
- From the postulates of Boolean algebra, it follows that the sum of two minterms in adjacent squares can be simplified to a single product term consisting of only two literals

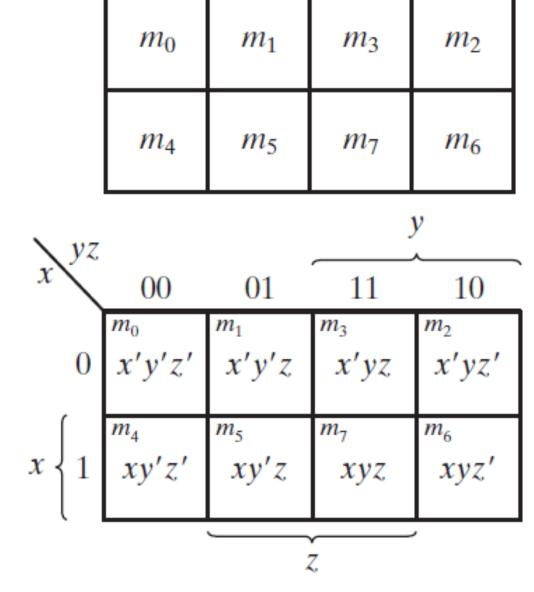


- Here is how we optimize the logic gate expression using maps:
- 1. We look for a cluster of adjacent squares with the function value being 1 (or true):
  - 1. A cluster of 8 squares (meaning the entire function is 1)
  - 2. A cluster of 4 squares (meaning one literal)
  - 3. A cluster of 2 squares (meaning two literals ANDed)
  - 4. A single square with all three variables ANDed (the minterm)
- 2. We OR all the expressions related to the clusters
- Note that "adjacent" squares mean vertically or horizontally, not diagonally

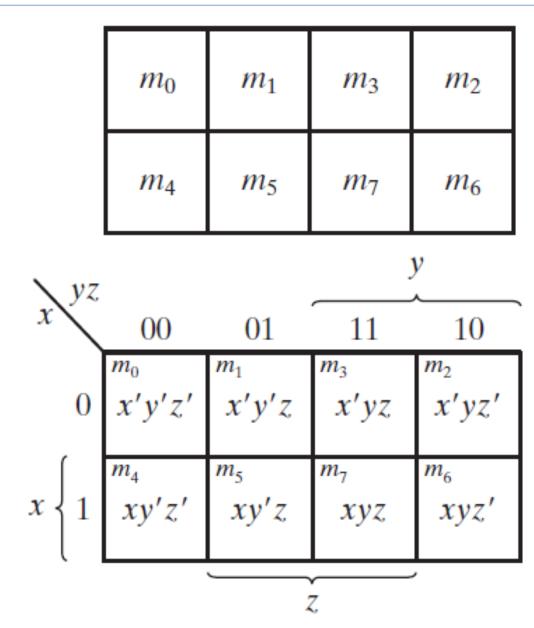

#### • Full adder:

Α	В	C <sub>o</sub>	C <sub>1</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

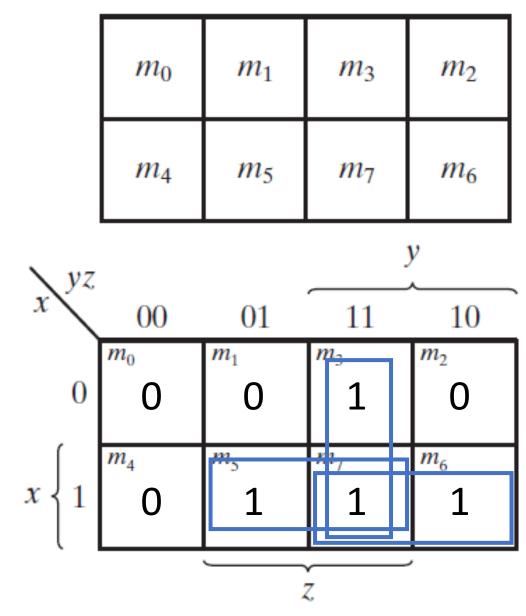- Three clusters of 2 squares
- Thus,  $C_1 = xy + yz + zx$  $C_1 = AB + BC_0 + C_0A$



• 
$$F(x, y, z) = \sum (1,2,3,5,7)$$

- We have one cluster of 4 squares
- This represents z
- One cluster of 2 squares
- This represents x'y
- Thus, F = z + x'y

